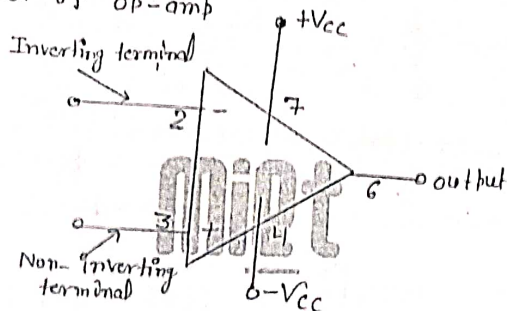



Operational amplifier (Op-amp) :

- Op-amp is a direct coupled high gain amplifier which can be used to amplify ac as well as dc signals.
- It is mainly used for mathematical operation like addition, subtraction, integration differentiation etc and hence named as operational amplifier.

Symbol of op-amp




Pin diagram of op-amp

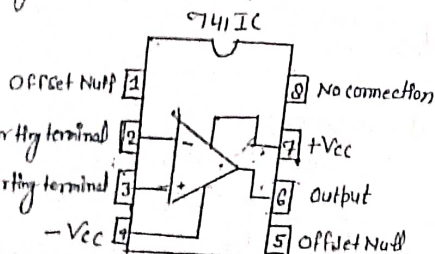

for offset null we use $10k\Omega$ resistance (as a potentiometer) between pin no. 1 & 5

Quest: What is op-amp. Draw its block diagram. Also show its equivalent circuit. (2015-16, 2017-18, 2020-21)

Ans:

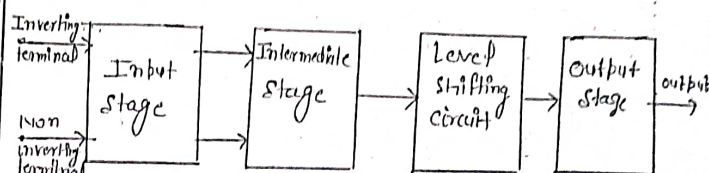

Input stage:

- The input stage is the dual input balance output (DIBO) differential amplifier.
- Its function is to amplify the difference between two input signals.
- It provides high differential gain, high input impedance.

Intermediate stage:

- The overall gain requirement of an op-amp is very high. Intermediate stage is used to provide the required additional gain.

- It consists of another differential amplifier with dual input and unbalanced (single ended) output.


Level shifting circuit:

- As the op-amp amplifies dc signal also, the small dc voltage level of previous stage may get amplified and applied as the input to the next stage causing distortion in the final output.
- So level shifting circuit is used to bring down the dc level to ground potential.

Output stage:

- It is the final stage which is usually consists of a push pull complementary amplifier.
- The output stage decreases the output impedance and increases the current supplying capability of the op-amp.

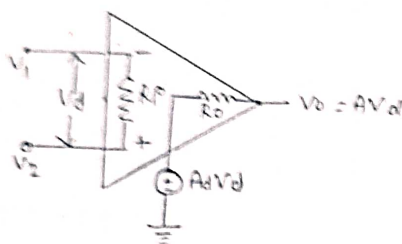
Equivalent circuit (Practical circuit) of op-amp




mode of operation (open loop) :-

1) Single Ended operation: Single ended input operation results when i/p signal is connected to one input with the other input connected to ground.

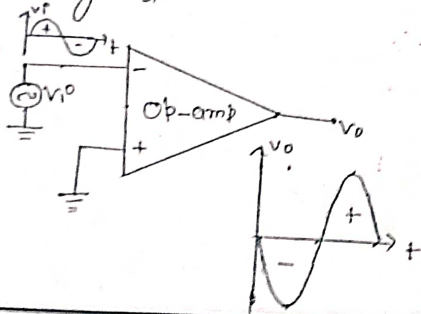
a) Inverting Amplifier: Input is applied at inverting terminal and non-inverting terminal is connected to ground.



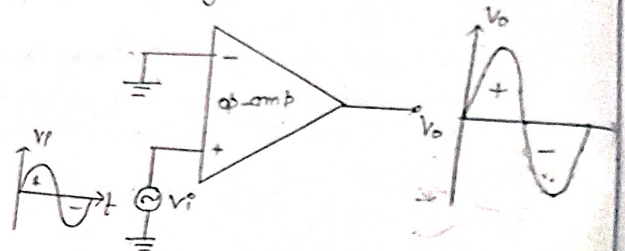ii) Non inverting amplifier: Input is applied at non inverting terminal and inverting terminal is connected to ground.



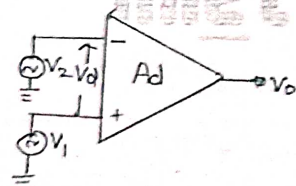Double ended Operation (Differential mode) :- when input signals are applied at both terminals then it is called differential mode.



for an ideal amplifier

$$V_o \propto (V_1 - V_2)$$

$$V_o = A_d (V_1 - V_2)$$

$$V_o = A_d V_d$$

Where

A_d : differential gain

V_d : difference in input voltage.

mode of same input is applied at both inputs i.e. $V_1 = V_2$ then ideally $V_o = 0$. But we get some value of V_o because of mismatch in internal circuitry.

So the output of practical differential

not only depends on difference voltage but also depends on the average common level of two input signals i.e. common mode signal (V_c).

Common mode o/p of op-amp is given as:

$$V_o = A_c V_c$$

A_c = common mode gain

$$V_c = \text{common mode voltage} = \frac{V_1 + V_2}{2}$$

The total output of any practical differential op-amp can be expressed as:


$$V_o = A_d V_d + A_c V_c$$

Ques 2: write short notes on the following:

- Input offset voltage
- Input offset current
- Input bias current


Ans 2: (i) Input offset voltage (V_{io}):

- In ideal op-amp, the output will be zero when both the input terminals are grounded.
- For practical op-amp it is found that output is not zero (called offset output voltage) if input is zero. This is due to imbalance present in the op-amp.
- An extra small amount of voltage is applied at any one of the input terminals to make the output voltage zero. This extra voltage is called input offset voltage (V_{io}).
- For ideal op-amp it is zero but for practical op-amp it is 2mV.

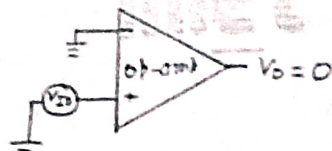

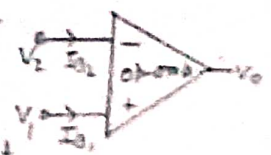(ii) Input offset current:

- The algebraic difference between the currents flowing into the non-inverting terminal and inverting terminal is called input offset current (I_{io}).
- In practice these currents are not equal because of imbalance present in the op-amp.



$$I_{io} = |I_{B1} - I_{B2}|$$


- For ideal op-amp it is zero but for practical op-amp it is 100nA.

(iii) Input bias current :-

- It is the average of currents flowing into the inverting and non inverting terminals.

- for ideal op-amp it is zero but for practical op-amp it is not

$$I_B = \frac{I_{B1} + I_{B2}}{2}$$

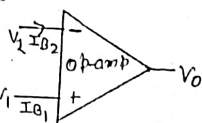

Ques 2 :- Define CMRR (common mode rejection ratio). (2015-16, 2020-21)

Ans. CMRR :- It is the ability of an op-amp to reject the common mode signal (noise) successfully. CMRR is defined as the ratio of differential mode gain (A_d) and common mode gain (A_c)

$$CMRR = \frac{A_d}{A_c}$$

For No noise (ideal op-amp) $A_c = 0$
So $CMRR = \infty$

for ideal op-amp CMRR is infinite but for practical op-amp it is 90 dB.

CMRR in dB:

$$CMRR = 20 \log_{10} \frac{A_d}{A_c}$$

Ques 3 :- Define slew rate. Also find the expression for maximum frequency. (2015-16)

Ans. Slew rate (SR) :- The slew rate is defined as the maximum rate of change in output voltage with respect to time.

$$SR = \left. \frac{\Delta V_O}{\Delta t} \right|_{\max} \quad (V/\mu s)$$

for ideal op-amp slew rate is infinite but for practical op-amp it is 0.5 V/ μ s.

If changes in o/p voltage are small then

$$SR = \left. \frac{dV_O}{dt} \right|_{\max} = \text{slope of signal}$$

for proper amplification:

$$SR \geq \left. \frac{dV_O}{dt} \right|_{\max}$$

Expression for maximum frequency :-
Let o/p voltage of op-amp is

$$V_O = V_m \sin \omega t$$

$$\frac{dV_O}{dt} = V_m \cos \omega t \times \omega$$

$$\left. \frac{dV_O}{dt} \right|_{\max} = \omega V_m = 2\pi f V_m \quad \text{--- (1)}$$

for proper amplification


$$SR \geq \left. \frac{dV_O}{dt} \right|_{\max}$$

$$SR \geq 2\pi f V_m$$

$$f \leq \frac{SR}{2\pi V_m}$$

$$f_{max} = \frac{SR}{2\pi V_m}$$

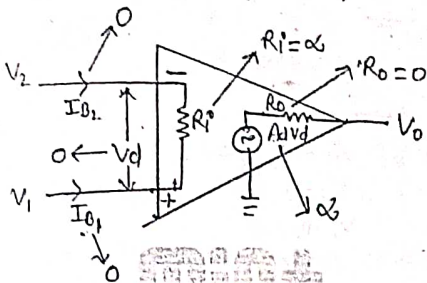Ques 4: Write the characteristics of ideal op-amp. (2016-17, 2017-18, 2020-21)



Characteristics:

1) Open loop gain should be infinite.

$$A_d (A_{VOL}) = \infty$$

2) Input resistance should be infinite.

$$R_i = \infty$$

3) Slew rate should be infinite.

$$SR = \infty$$

4) CMRR should be infinite.

$$CMRR = \infty$$

5) Input offset voltage should be zero.

$$V_{IO} = 0$$

6) Input offset current should be zero.

$$I_{IO} = 0$$

7) Input bias current should be zero.


$$I_B = 0$$

Ques 5: Compare ideal and practical op-amp.

Ans: Ideal op-amp vs practical op-amp.

SN.	Parameters	Ideal Value	Practical Value
1.	CMRR	∞	90dB
2.	Slew rate	∞	0.5V/μs
3.	Open loop voltage gain	∞	10^5
4.	Input resistance	∞	2MΩ
5.	Output resistance	0	75Ω
6.	Input offset voltage	0	2mV
7.	Input offset current	0	20nA
8.	Input bias current	0	80nA

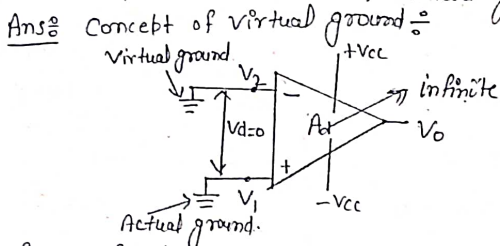Ques: 1 Explain the concept of virtual ground.




- For an ideal op-amp $A_d = \infty$
 $V_o = A_d V_d$
 $V_d = \frac{V_o}{A_d}$
 $V_d = \frac{V_o}{\infty} = 0$
 So $V_1 - V_2 = 0$
 $V_1 = V_2$
- If one terminal of op-amp is connected to ground then other terminal will also be at ground. This is called concept of virtual ground.

• Concept of virtual ground is used to determine closed loop voltage gain and output voltage.

Ques 2: Explain the inverting amplifier and derive the expression for closed loop voltage gain. (2015-16, 2016-17, 2017-18)

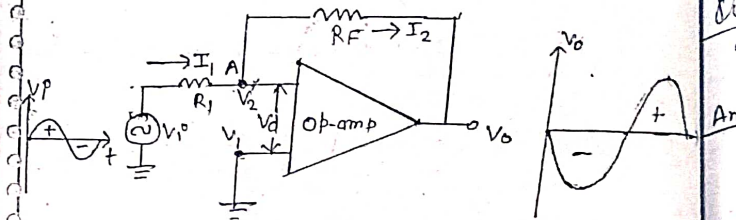Ans: Inverting amplifier: An op-amp circuit that produce an amplified output signal that is 180° out of phase with input signal.



Expression for output voltage:

Here $V_1 = 0$ --- 1

From concept of virtual ground

$$V_d = 0$$

$$V_1 - V_2 = 0$$

$$V_1 = V_2$$

$$\text{But } V_1 = 0$$

$$\text{So } V_2 = 0 \text{ --- 2}$$

Applying KCL at Node A

$$I_1 = I_2$$

$$\frac{V_1 - V_2}{R_1} = \frac{V_2 - V_o}{R_F}$$

$$\text{But } V_2 = 0$$


$$\frac{V_1}{R_1} = -\frac{V_o}{R_F}$$

$$A_v = \frac{V_o}{V_1} = -\frac{R_F}{R_1}$$

- The negative sign denotes a 180° phase difference between input and output.
- Gain can be set to any value by manipulating the value of R_F and R_1 .

Ques 2 :- Explain the working of non inverting amplifier. Also derive the expression for output voltage. (2013-14, 2017-18)

Ans: Non inverting amplifier.

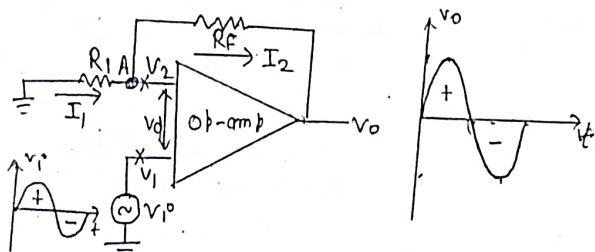

A non-inverting amplifier is an op-amp circuit design to provide positive voltage gain. The input is directly applied to non inverting terminal. Expression for output voltage :-

Here $V_i = V_p$ ----- (1)

From concept of virtual ground

$$V_d = 0$$

$$V_1 - V_2 = 0$$

$$V_1 = V_2$$

But $V_1 = V_i$

So $V_2 = V_p$ ----- (2)

Applying KCL at Node A.

$$I_1 = I_2$$

$$\frac{0 - V_2}{R_1} = \frac{V_2 - V_o}{R_F}$$

But $V_2 = V_p$

$$-\frac{V_i}{R_1} = \frac{V_p}{R_F} - \frac{V_o}{R_F}$$

$$\frac{V_o}{R_F} = \frac{V_p}{R_F} + \frac{V_i}{R_1}$$


$$\frac{V_o}{V_p} = \frac{R_F}{R_F} + \frac{R_F}{R_1}$$

$$A_v = \frac{V_o}{V_i} = 1 + \frac{R_F}{R_1}$$

- The positive sign denotes that input and output are in same phase.
- Gain can be set to any value by manipulating the value of R_F and R_1 .

Ques 3 :- Draw the circuit of op-amp as voltage follower and find the expression for voltage gain. (2016-17)

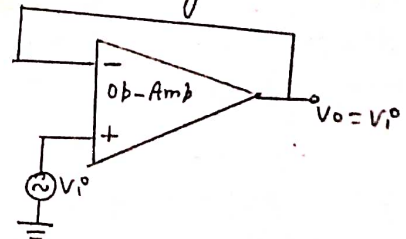Ans: Voltage follower or unit gain :- In voltage follower output voltage follows the input voltage i.e. $V_o = V_i$. Closed loop voltage gain of this circuit is 1. It has high input impedance and low output impedance, so used for impedance matching.



$$A_v = 1 \text{ [requirement]}$$

Gain of non inverting amplifier is given as:

$$A_v = 1 + \frac{R_F}{R_1}$$

Let $R_F = 0$ & $R_1 = \infty$

$$A_v = 1 + \frac{0}{\infty}$$


$$[A_v = 1] \text{ [unity gain amplifier]}$$

$$\frac{V_o}{V_P} = 1$$

$$[V_o = V_P] \text{ [voltage follower]}$$

Ques 4: Explain summing or adder amplifier using ideal op-amp (2015-16).

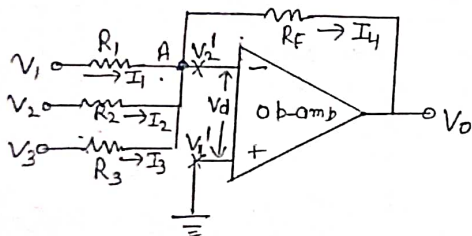Ans: Summing amplifier: summing amplifier is an op-amp circuit, which can accept two more inputs and produces output as the sum of these inputs.



Expression for output voltage

Here $V_1' = 0$ ----- 1

from concept of virtual ground
 $V_d = 0$

$$V_1' - V_2' = 0$$

$$V_1' = V_2'$$

but $V_2' = 0$

So $V_1' = 0$ ----- 2

Applying KCL at Node A

$$I_1 + I_2 + I_3 = -I_4$$

$$\frac{V_1 - V_1'}{R_1} + \frac{V_2 - V_2'}{R_2} + \frac{V_3 - V_2'}{R_3} = \frac{V_2' - V_o}{R_F}$$

But $V_2' = 0$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_o}{R_F}$$

$$V_o = - \left[\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right]$$

a) If $R_1 = R_2 = R_3 = R$

then $V_o = -\frac{R_F}{R} [V_1 + V_2 + V_3]$

So ckt works as summing amplifier

b) If R_1, R_2, R_3

then $V_o = -[V_1 + V_2 + V_3]$

So ckt works as a summer ckt.


c) If $R_1 = R_2 = R_3 = 3R_F$

then $V_o = \frac{V_1 + V_2 + V_3}{3}$

So ckt works as an average circuit.

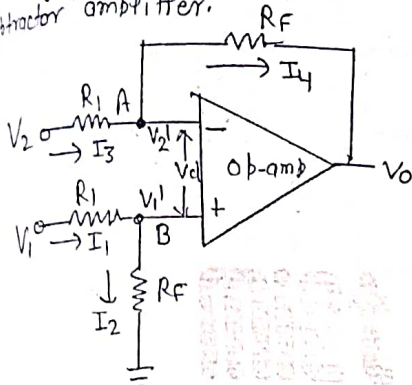Q.5: Draw and explain the difference amplifier. (2016-17).
 Difference or subtractor amplifier

A circuit that amplifies the difference between two input signals is called difference amplifier or subtractor amplifier.



Expression for output voltage

Applying KCL at Node B

$$I_1 = I_2$$

$$\frac{V_1 - V_1'}{R_1} = \frac{V_1' - 0}{R_F}$$

$$\frac{V_1}{R_1} = \frac{V_1'}{R_F} + \frac{V_1'}{R_1}$$

$$\frac{V_1}{R_1} = V_1' \left(\frac{R_1 + R_F}{R_F R_1} \right)$$

$$V_1' = \left(\frac{R_F}{R_1 + R_F} \right) \cdot V_1 \quad \text{--- 1}$$

from concept of virtual ground

$$V_d = 0$$

$$V_1' - V_2' = 0$$

Applying KCL at Node A

$$I_3 = I_4$$

$$\frac{V_2 - V_2'}{R_1} = \frac{V_2' - V_o}{R_F}$$

$$\frac{V_2}{R_1} - \frac{V_2'}{R_1} = \frac{V_2'}{R_F} - \frac{V_o}{R_F}$$

$$\frac{V_o}{R_F} = \frac{V_2'}{R_F} + \frac{V_2'}{R_1} - \frac{V_2}{R_1}$$

$$\frac{V_o}{R_F} = V_2' \left(\frac{R_1 + R_F}{R_1 R_F} \right) - \frac{V_2}{R_1}$$

$$\text{But } V_1' = V_2'$$

$$\frac{V_o}{R_F} = \left(\frac{R_F}{R_1 + R_F} \right) \cdot V_1 \left(\frac{R_1 + R_F}{R_1 R_F} \right) - \frac{V_2}{R_1}$$

$$V_o = \frac{R_F}{R_1} [V_1 - V_2]$$

So ckt works as a difference amplifier or subtractor amplifier


if $R_1 = R_F$

$$V_o = V_1 - V_2$$

So ckt works as a difference or subtractor.

Ques-1 Draw the circuit of an integrator using op-amp and explain its working (2016-17, 2017-18).

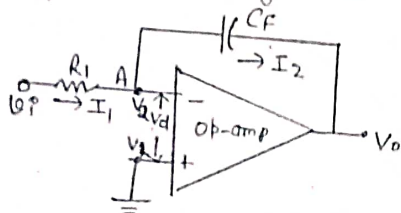Ans: Integrator: A circuit that performs the integration of input signal is called integrator circuit.



Expression for output voltage:

Here $V_1 = 0$

From concept of virtual ground - 1

$$V_d = 0$$

$$V_1 = V_2$$

$$\text{but } V_1 = 0$$

$$\text{So } V_2 = 0$$

$$I_1 = I_2 \quad \text{--- 2}$$

Applying KCL at Node A

$$I_1 = I_2$$

$$\frac{V_i - V_2}{R_1} = C_f \frac{d(V_2 - V_o)}{dt}$$

$$\text{but } V_2 = 0$$

$$\frac{V_i}{R_1} = C_f \frac{d(-V_o)}{dt}$$

$$dV_o = -\frac{1}{R_1 C_f} V_i dt$$

Now applying integration on both side


$$\int dV_o = \int -\frac{1}{R_1 C_f} V_i dt$$

$$V_o = -\frac{1}{R_1 C_f} \int_0^t V_i dt$$

$$V_o \propto \int_0^t V_i dt$$

Since output voltage is directly proportional to the integral of input signal, hence circuit is called integrator circuit.

Output wave for square input:

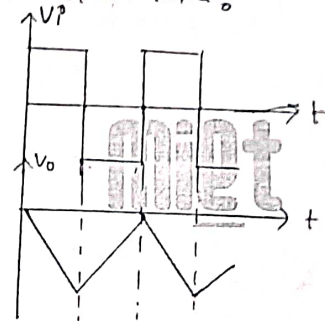


Application:

- It is used for generating triangular wave.
- It is used in digital to analog converter circuit.
- It is used as low pass filter.

Ques 2: Draw the circuit diagram of differentiator using op-amp and explain its working. (2015-16, 2017-18, 2020-21)

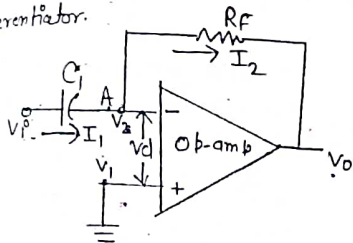Ans: Differentiator: A circuit that performs the mathematical differentiation of input signal is called differentiator.



Expression for output voltage:

Here $V_1 = 0$

from concept of virtual ground

$$V_1 = 0$$

$$V_1 - V_2 = 0$$

$$V_1 = V_2$$

$$\text{but } V_1 = 0$$

$$\text{So } V_2 = 0 \quad \dots \quad 2$$

Applying KCL at Node A

$$I_1 = I_2$$

$$C \frac{d(V_i - V_2)}{dt} = \frac{V_2 - V_o}{R_F}$$

$$\text{but } V_2 = 0$$


$$C \frac{dV_i}{dt} = -\frac{V_o}{R_F}$$

$$V_o = -R_F C \frac{dV_i}{dt}$$

$$V_o \propto \frac{dV_i}{dt}$$

Since output voltage is directly proportional to the differentiation of input signal, so circuit is called differentiator circuit.

Output for triangular input wave:

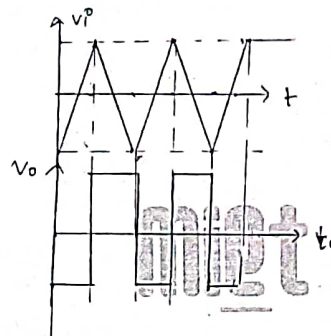

Application:

- It is used to generate square wave.
- It is also used in analog to digital converter circuit.
- It is used as high pass filter.

Ques 3: Write short notes on comparator.


Ans: Comparator: Comparator is a circuit which

compares signal voltage applied at one terminal of op-amp with reference voltage applied at another terminal.

Comparator produces high (+V_{sat}) or low (-V_{sat}) output depending which input is higher. It is also called

Voltage Comparator. Comparator are of two types.

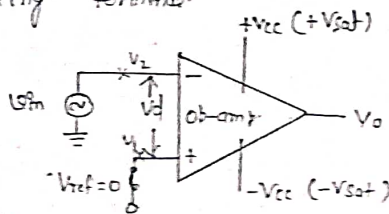- i) Inverting comparator (ii) Non-Inverting comparator
- ii) Inverting comparator (inverting zero crossing detector):
In inverting comparator input is applied at inverting terminal and reference voltage is applied at non-inverting terminal.



Working principle:

- During the positive half cycle of input signal, the voltage at the inverting terminal is greater than zero. So, output of the inverting comparator will be equal to $-V_{sat}$.

$$V_d = V_1 - V_2$$

$$= 0 - V_{in}$$

$$= -V_c$$



$$V_o = A_{OL} \times V_d$$

$$= -V_{sat}$$

- During the negative half cycle of input signal, the voltage at the inverting terminal is less than zero. So, output of the inverting comparator will be equal to $+V_{sat}$.

$$V_d = V_1 - V_2$$

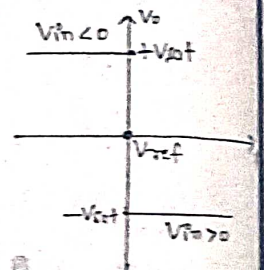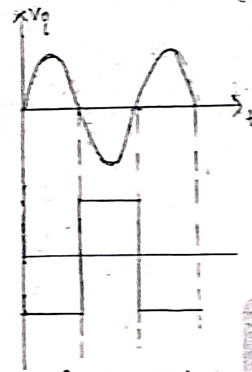
$$\begin{aligned} &= 0 - (-V_{in}) \\ &= +V_c \\ V_o &= A_{OL} \times V_d \\ &= +V_{sat} \end{aligned}$$



Input output characteristics

Transfer characteristics

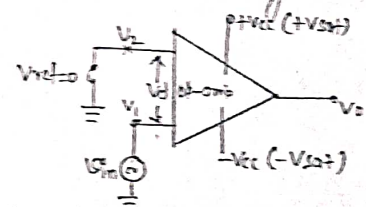- ii) Non-Inverting Comparator: In non-inverting comparator input is applied at non-inverting terminal and reference voltage is applied at inverting terminal.



Working principle:

- During positive half cycle of input signal the voltage at the non-inverting terminal is greater than zero. So,

Output of the non-inverting comparator will be $\pm V_{sat}$

$$V_d = V_1 - V_2$$

$$= V_{in} - 0$$

$$= +V_e$$

$$V_o = A_{OL} \times V_d$$

$$= +V_{sat}$$

During the negative half cycle of input signal the voltage present at the non-inverting terminal is less than zero. So the output of non-inverting comparator will be $-V_{sat}$.



$$V_d = V_1 - V_2$$

$$= -V_{in} - 0$$

$$= -V_e$$

$$V_o = A_{OL} \times V_d$$

$$= -V_{sat}$$

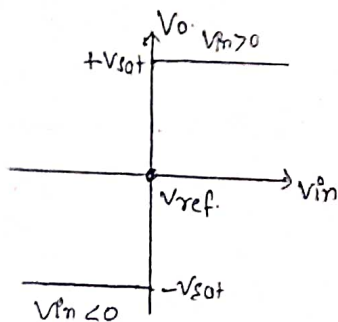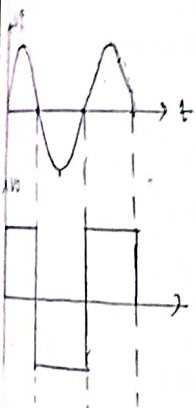

Transfer characteristics

Input output characteristics

Ques-1 An operational amplifier has a differential gain of 10^3 and CMRR of 100, input voltages are 120 μ V and 80 μ V. Define the output voltage. (2017-18)

Ans: $CMRR = \frac{A_d}{A_c}$
 $A_c = \frac{10^3}{100} = 10$

$$V_o = A_d V_d + A_c V_c$$

$$= 10^3 (V_1 - V_2) + 10 \left(\frac{V_1 + V_2}{2} \right)$$

$$= 10^3 (120 - 80) \times 10^{-6} + 10 \left(\frac{120 + 80}{2} \right) \times 10^{-6}$$

$$= 40 \times 10^{-3} + 10^{-3}$$

$$= 41 \text{ mV}$$

Ques-2 An operational amplifier has differential gain of 10^2 and CMRR of 80 dB. Input voltages are 100 μ V and 60 μ V. Find output voltage. (2015-17).

Soln: $CMRR = 20 \log \left| \frac{A_d}{A_c} \right|$
 $80 = 20 \log \left| \frac{10^2}{A_c} \right|$
 $4 = \log \left| \frac{10^2}{A_c} \right|$

Taking anti log we get

$$10^4 = 10^2 / A_c$$

$$A_c = 10^{-2}$$


$$V_o = A_d V_d + A_c V_c = A_d (V_1 - V_2) + A_c \left(\frac{V_1 + V_2}{2} \right)$$

$$= 10^2 (100 - 60) \times 10^{-6} + 10^{-2} \left(\frac{100 + 60}{2} \right) \times 10^{-6}$$

$$= 10^2 \times 40 \times 10^{-6} + 80 \times 10^{-8}$$

$$\approx 4 \text{ mV}$$

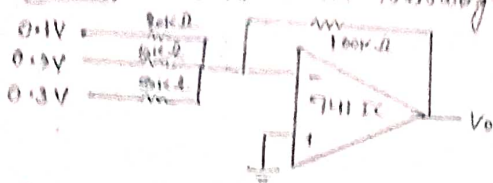Ques 3: Find V_o for the following circuit (2009-10, 2010-11).




Soln: It is adder amplifier circuit.

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$= - \left[\frac{100}{10} \times 0.1 + \frac{100}{10} \times 0.2 + \frac{100}{10} \times 0.3 \right]$$

$$= -3.1 \text{ V}$$

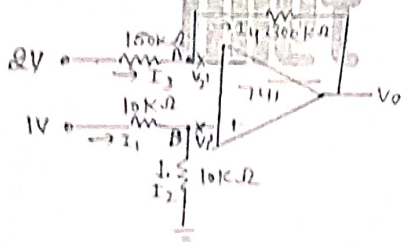Ques 4: Find the output voltage for the following circuit (2017-18).



Soln: Let voltage at Node B is V_1

Applying KCL at Node B

$$I_1 = I_2$$

$$\frac{1 - V_1}{10} = \frac{V_1 - 0}{10}$$

$$V_1 = 0.5 \text{ V}$$

From concept of virtual ground voltage at node A is 0.5V

Now Applying KCL at node A


B. Tech 1 Year [Subject Name: Electronics Engineering]

$$\frac{2 - 0.5}{150} = \frac{0.5 - V_o}{300}$$

$$1.5 = \frac{0.5 - V_o}{2}$$

$$V_o = -2.5 \text{ V}$$

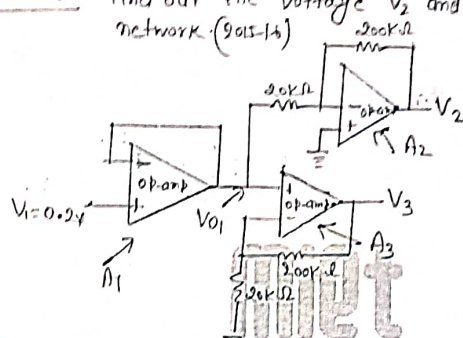Ques 5: Find out the voltage V_2 and V_3 of the following network (2015-16)



Soln: op-amp A₁ is voltage follower so $V_{o1} = V_{in} = 0.2 \text{ V}$

op-amp A₂ is inverting amplifier.

$$V_2 = - \frac{R_f}{R_i} \times V_p$$

$$= - \frac{100}{20} \times 0.2 \text{ V}$$

$$V_2 = -2 \text{ V}$$


op-amp A₃ is non-inverting amplifier

$$V_3 = \left(1 + \frac{R_f}{R_i} \right) \times V_p$$

$$= \left(1 + \frac{100}{20} \right) \times 0.2 \text{ V}$$

$$V_3 = 2.2 \text{ V}$$

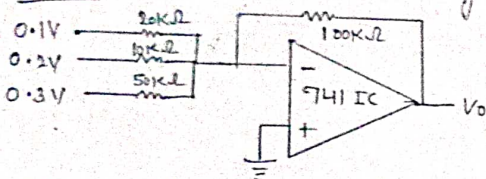Ques 3: Find V_o for the following circuit (2009-10, 2010-19).




Soln: It is adder amplifier circuit.

$$V_o = - \left[\frac{R_F}{R_1} \cdot V_1 + \frac{R_F}{R_2} \cdot V_2 + \frac{R_F}{R_3} \cdot V_3 \right]$$

$$= - \left[\frac{100}{20} \times 0.1 + \frac{100}{10} \times 0.2 + \frac{100}{50} \times 0.3 \right]$$

$$= -3.1 \text{ V}$$

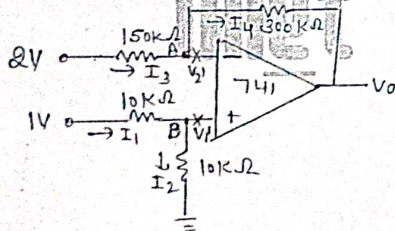Ques 4: Find the output voltage for the following circuit (2017-18).



Soln: Let voltage at Node B is V_1 .
Applying KCL at Node B

$$I_1 = I_2$$

$$\frac{1 - V_1}{10} = \frac{V_1 - 0}{10}$$

$$V_1 = 0.5 \text{ V}$$


From concept of virtual ground voltage at node A is 0.5V
Now Applying KCL at node A

$$\frac{2 - 0.5}{150} = \frac{0.5 - V_o}{300}$$

$$1.5 = \frac{0.5 - V_o}{2}$$

$$V_o = -2.5 \text{ V}$$

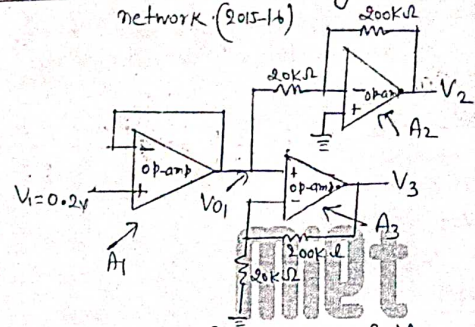Ques 5: Find out the voltage V_2 and V_3 of the given network (2015-16)



Soln: op-amp A₁ is voltage follower so
 $V_{o1} = V_{in}$
 $= 0.2 \text{ V}$

op-amp A₂ is inverting amplifier.

$$\text{So } V_2 = - \frac{R_F}{R_1} \times V_P$$

$$= - \frac{200}{20} \times 0.2 \text{ V}$$

$$V_2 = -2 \text{ V}$$


op-amp A₃ is non-inverting Amplifier

$$\text{So } V_3 = \left(1 + \frac{R_F}{R_1} \right) \cdot V_P$$

$$= \left(1 + \frac{200}{20} \right) \times 0.2 \text{ V}$$

$$V_3 = 2.2 \text{ V}$$

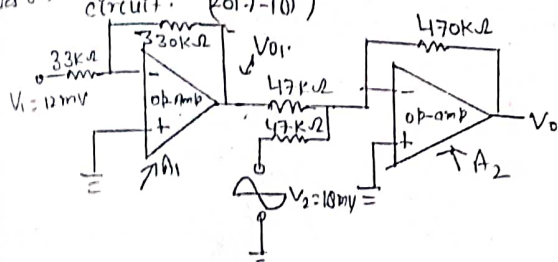Ques 6: Find the output voltage for the following circuit. (2017-18)



Soln: op-amp A1 is inverting amplifier. so output of op-amp A1 is

$$V_{01} = -\left(\frac{R_F}{R_1}\right) \times V_P$$

$$= -\frac{330}{33} \times 12 \text{ mV}$$

$$= -120 \text{ mV}$$

op-amp A2 is adder circuit. so output of op-amp A2 is

$$V_0 = -\left[\frac{R_F}{R_1} \times V_1 + \frac{R_F}{R_2} \times V_2\right]$$

$$= -\left[\frac{470}{47} \times (-120 \text{ mV}) + \frac{470}{47} \times 18 \text{ mV}\right]$$

$$= -[-1200 \text{ mV} + 1800 \text{ mV}]$$

$$= 1020 \text{ mV}$$

$$= 1.02 \text{ V}$$

Ques 7: for an op-amp having a slew rate of $2.4 \text{ V}/\mu\text{s}$, what is the maximum closed loop voltage gain that can be used when the input signal varies $\pm 10 \text{ mV}$. (2014-15)

Soln: given $\Delta t = 10 \mu\text{s} = 10 \times 10^{-6} \text{ s}$

$$SR = 2.4 \text{ V}/\mu\text{s} = 2.4 \times 10^6 \text{ V/s}$$

$$\text{Now } SR = \frac{\Delta V_0}{\Delta t}$$


$$\text{but } \Delta V_0 = A_{CL} \times \Delta V_P$$

$$\text{So } SR = \frac{A_{CL} \times \Delta V_P}{\Delta t}$$

$$2.4 \times 10^6 = \frac{A_{CL} \times 0.3}{10 \times 10^{-6}}$$

$$A_{CL} = 80$$

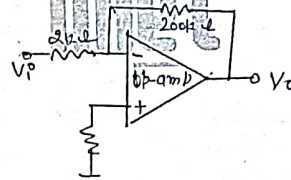Ques 8: for an input of $V_P = 5 \text{ mV}$ in the given circuit, determine the maximum frequency that can be used. The op-amp has a slew rate of $0.4 \text{ V}/\mu\text{s}$. (2010-19).



Soln: given $V_P = 5 \text{ mV}$, $SR = 0.4 \text{ V}/\mu\text{s} = 0.4 \times 10^6 \text{ V/s}$

$$\text{Now } V_0 = -\frac{R_F}{R_1} \times V_P = -\frac{200}{2} \times 5 \times 10^{-3} = -5 \text{ V}$$

so $V_m = 5 \text{ V}$ (maximum voltage at o/b)

$$f_{max} = \frac{SR}{2\pi V_m} = \frac{0.4 \times 10^6}{2\pi \times 5}$$

$$f_{max} = 12.732 \text{ KHz}$$

Q. Determine the output voltage of an OP-Amp for the input voltage of $V_1 = 150\mu V$ and $V_2 = 140\mu V$. The amplifier has differential gain $A_d = 4000$ and CMRR is 100. (2021-22 odd)

Sol: Given: $V_1 = 150\mu V$ $A_d = 4000$
 $V_2 = 140\mu V$ CMRR = 100

we know that CMRR = $\frac{A_d}{A_c} \Rightarrow A_c = \frac{A_d}{CMRR} = \frac{4000}{100} = 40 \Rightarrow A_c = 40$


$V_d = V_1 - V_2$ $V_c = \frac{V_1 + V_2}{2} = \frac{150 + 140}{2} = 145\mu V$

$= 150 - 140 = 10\mu V$

Now, $V_o = A_d V_d + A_c V_c$
 $= (4000)(10\mu V) + (40)(145\mu V)$
 $= 40,000\mu V + 5800\mu V$
 $= 45800\mu V$

$V_o = 45.8mV$ Ans

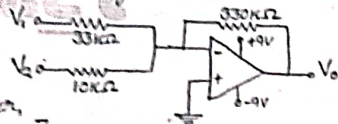Q. Determine the output of the following circuit. (2021-22 odd)
 Given $V_1 = V_2 = 0.15V$



Sol: It is an example of inverting summing amplifier.

$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right]$

$= - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right]$

$= - \left[\frac{330k\Omega}{33k\Omega} \times 0.15V - \frac{330k\Omega}{10k\Omega} \times 0.15 \right]$

$= -1.5V - 4.95V$

$V_o = -6.45$ Ans.

Q. Explain the concept of Virtual ground in OP-Amp. Determine output voltage for given network. (2021-22 even)

Sol: Apply KCL at node A


$\frac{2V - V_A}{2k\Omega} + \frac{4V - V_A}{2k\Omega} = 0$

$2V - V_A + 4V - V_A = 0$

$2V_A = 8V \Rightarrow V_A = 4V$

Now, $V_o = \left(1 + \frac{R_f}{R_i} \right) V_A = \left(1 + \frac{6k\Omega}{2k\Omega} \right) 4V = 4 \times 4V = 16V$

$V_o = 16V$ Ans.

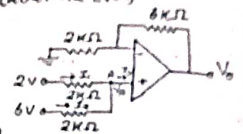

Q. Determine the output voltage of following circuit. (2021-22 Even)

Sol: Apply KCL at node-A

$I_1 = I_2$

$\frac{11V - V_A}{20k\Omega} = \frac{V_A - 0}{20k\Omega}$

$11V - V_A = V_A$

$2V_A = 11V \Rightarrow V_A = 5.5V$


Now due to Virtual ground $V_A = V_B = 5.5V$

Apply KCL at node-B


$\frac{7V - 5.5V}{100k\Omega} = \frac{5.5V - V_o}{100k\Omega}$

$1.5V = 5.5V - V_o$

$V_o = 4V$ Ans.

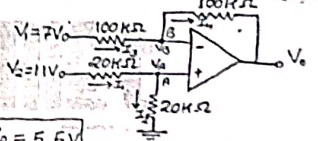

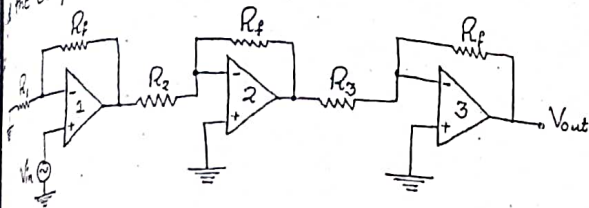Q. Shows the multi-stage OP-Amp Circuit. The resistor values are: $R_f = 470K\Omega$; $R_1 = 4.3K\Omega$; $R_2 = 33K\Omega$ and $R_3 = 33K\Omega$. Find the output voltage for an input of $80\mu V$.



Given: $R_f = 470K\Omega$
 $R_1 = 4.3K\Omega$ $V_{in} = 80\mu V$
 $R_2 = 33K\Omega$
 $R_3 = 33K\Omega$

Stage gain of first stage, $A_1 = 1 + (R_f/R_1) = 1 + (470K\Omega/4.3K\Omega) = 110.3$

Stage gain of second stage, $A_2 = -R_f/R_2 = -470K\Omega/33K\Omega = -14.2$

Stage gain of third stage, $A_3 = -R_f/R_3 = -470K\Omega/33K\Omega = -14.2$

Overall Voltage gain, $A = A_1 A_2 A_3 = (110.3) \times (-14.2) \times (-14.2) = 22240.89$

Output Voltage, $V_{out} = A \times V_{in} = 22240.89 \times 80\mu V = 1.78V$

$V_{out} = 1.78V$ Ans

Q. Two voltages of $+0.6V$ and $-1.4V$ are applied to the two input terminals of a summing amplifier. The respective input resistors are $400K\Omega$ and $100K\Omega$ and feedback resistor is $200K\Omega$. Determine the output voltage.

Q. The output voltage of the summing amplifier is given by:

$V_{out} = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$

Here $R_f = 200K\Omega$, $R_1 = 400K\Omega$, $R_2 = 100K\Omega$, $V_1 = +0.6V$, $V_2 = -1.4V$

$V_{out} = -200K\Omega \left(\frac{0.6}{400K\Omega} + \frac{-1.4}{100K\Omega} \right) = 2.5V$

$V_{out} = 2.5V$ Ans

Q. A differential amplifier has an output of $1V$ with a differential input of $10mV$ and an output of $5mV$ with a common-mode input of $10mV$. Find the CMRR in dB.


Sol: Differential gain, $A_{dm} = \frac{1V}{10mV} = 100$

Common-mode gain, $A_{cm} = \frac{5mV}{10mV} = 0.5$

$CMRR_{dB} = 20 \log_{10}(100/0.5) = 46dB$

$CMRR_{dB} = 46dB$ Ans

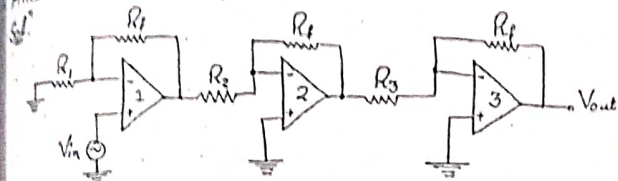Q1. Figure shows the multi-stage OP-Amp Circuit. The resistor values are: $R_1 = 470\text{K}\Omega$; $R_i = 4.3\text{K}\Omega$; $R_2 = 33\text{K}\Omega$ and $R_3 = 33\text{K}\Omega$. Find the output voltage for an input of $80\mu\text{V}$.



Given:- $R_1 = 470\text{K}\Omega$
 $R_i = 4.3\text{K}\Omega$ $V_{in} = 80\mu\text{V}$
 $R_2 = 33\text{K}\Omega$
 $R_3 = 33\text{K}\Omega$

Voltage gain of first stage, $A_1 = 1 + (R_1/R_i) = 1 + (470\text{K}\Omega/4.3\text{K}\Omega) = 110.3$

Voltage gain of second stage, $A_2 = -R_i/R_2 = -470\text{K}\Omega/33\text{K}\Omega = -14.2$

Voltage gain of third stage, $A_3 = -R_i/R_3 = -470\text{K}\Omega/33\text{K}\Omega = -14.2$

∴ Overall Voltage gain, $A = A_1 \cdot A_2 \cdot A_3 = (110.3) \times (-14.2) \times (-14.2) = 22240.89$

Output Voltage, $V_{out} = A \times V_{in} = 22240.89 \times 80\mu\text{V} = 1.78\text{V}$

$V_{out} = 1.78\text{V}$ Ans

Q2. Two voltages of $+0.6\text{V}$ and -1.4V are applied to the two input resistors of a summing amplifier. The respective input resistors are $400\text{K}\Omega$ and $100\text{K}\Omega$ and feedback resistor is $200\text{K}\Omega$. Determine the output voltage.

Sol:- The output voltage of the summing amplifier is given by:

$$V_{out} = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

Hence $R_f = 200\text{K}\Omega$, $R_1 = 400\text{K}\Omega$, $R_2 = 100\text{K}\Omega$, $V_1 = +0.6\text{V}$, $V_2 = -1.4\text{V}$

$$V_{out} = -200\text{K}\Omega \left(\frac{0.6}{400\text{K}\Omega} + \frac{-1.4}{100\text{K}\Omega} \right) = 2.5\text{V}$$

$V_{out} = 2.5\text{V}$ Ans

Q3. A differential amplifier has an output of 1V with a differential input of 10mV and an output of 5mV with a common-mode input of 10mV . Find the CMRR in dB.



Sol:- Differential gain, $A_{dm} = \frac{1\text{V}}{10\text{mV}} = 100$

Common-mode gain, $A_{cm} = \frac{5\text{mV}}{10\text{mV}} = 0.5$





$$\text{CMRR}_{\text{dB}} = 20 \log_{10} (100/0.5) = 46\text{dB}$$

$\text{CMRR}_{\text{dB}} = 46\text{dB}$ Ans

B. Tech I Year [Subject Name: Electronics Engineering]

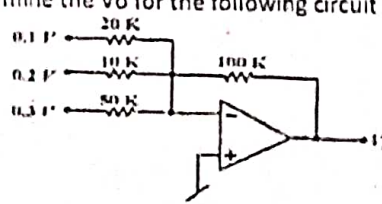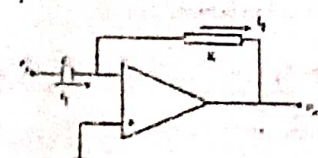5 Years AKTU University Examination Questions			
S. No	Questions	Unit-3	
		Session	Lecture No
1	What is an op amp ? How it is used as an integrator and summer ?	2009-10(2)	22-27
2	Enlist the Characteristics of an ideal op amp. Draw the subtractor using op-amp and explain its working	2009-10(1)	22-27
3	(i) What is an operational amplifier? Draw its block diagram. Write the characteristics of an ideal operational amplifier. (ii) With help of the circuit diagram, explain the working of OPAMP as differentiator	2020-21(1) 2019-20(1)	22-27
4	Enlist the characteristics of an Ideal OPAMP.	2013-14(1)	22-27
5	Draw the circuit diagram for unity gain amplifier. Where is it used and why ?	2009-10(2)	22-27
6	Write short note on Non Inverting Amplifier	2013-14(1) 2014-15(1)	22-27
7	Draw the circuit of subtractor using op Amp and explain its working. Also obtain expression for its output	2019-20(1) 2014-15(1)	22-27
8	Draw the circuit of integrator using op Amp and explain its working. Also obtain expression for its output.	2019-20(1) 2017-18(2)	22-27
9	Draw the op-amp based circuit to give: $V_o = V_1 + V_2 + V_3$	2009-10(1)	22-27
10	Determine the V_o for the following circuit 	2009-10(1)	22-27
11	An ideal operational amplifier is used to make an inverting amplifier. There are two input terminals of the operational amplifier and are at the same potential because: (a) The two inputs are directly short circuited internally (b) The resistance of operational amplifier is infinity (c) The open loop gain of the operational amplifier is unity (d) All the above except option (a)	2009-10(1)	22-27
12	For the circuit shown in the Fig. The output voltage V_o is given by  Figure-1 (i) $V_o = -\frac{1}{RC} \frac{dV_i(t)}{dt}$ (ii) $V_o = -\frac{1}{RC} \int V_i(t) dt$ (iii) $V_o = -RC \frac{dV_i(t)}{dt}$ (iv) $V_o = -RC \int V_i(t) dt$	2009-10(2)	22-27

B. Tech 1 Year [Subject Name: Electronics Engineering]

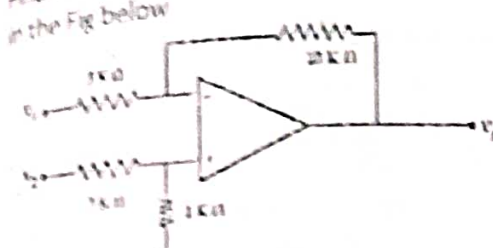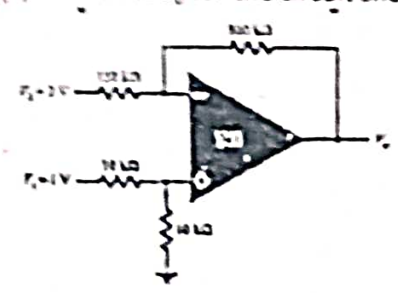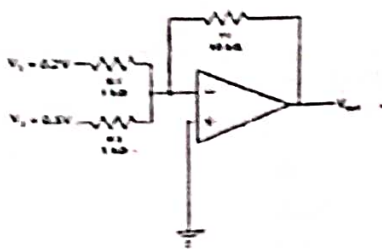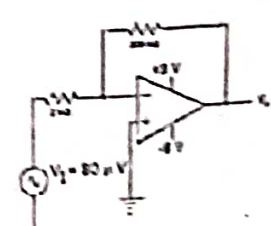13	Find the output voltage of the following op-amp circuit shown in the Fig below 	2009-10(2)	22-27
14	The output voltage in op amp differentiator with input voltage V_i the output voltage is given bywhen $R=1k$ and $C=1pf$	2010-11(2)	22-27
15	A sinusoidal signal with peak value 6 mV and 2 KHz frequency is applied to the input of an ideal OP-AMP Integrator with $R_a = 100K$ ohm and $C_i = 1\mu F$. Find the output voltage	2010-11(2)	22-27
16	(i) Determine the output voltage of an op-amp for input voltages of $V_{i1} = 100V$ and $V_{i2} = 120V$. The amplifier has a differential gain of $A_d = 4000$ and the value of CMRR is: (a) 150 (b) 10^3 (ii) Find V_o for the circuit shown below in Figure 6  Figure 6	2015-16(1)	22-27
17	Determine the output for the following circuits: (i)  (ii) 	2020-21(1)	22-27
18	(i) What do you mean by IOT? Discuss its various components. (ii) Define the following terms: (1) CMRR (2) Peak Inverse Voltage	2020-21(1)	22-27
19	State the basic difference between Bluetooth and Wi-Fi technology	2020-21(1)	22-27